

4TH SEM./ECE/ETC/2022(S)

Th-4 Analog Electronics and Linear IC

Full Marks: 80

Time- 3 Hrs


Answer any five Questions including Q No.1& 2
Figures in the right hand margin indicates marks

1. Answer **All** questions 2 x 10
 - a. Define Ripple factor. Mention ripple factor of half wave rectifier and full wave rectifier.
 - b. Define α and β of a transistor.
 - c. List different types of power amplifiers.
 - d. Write the full form of CMOS and draw it's symbol indicating each terminal.
 - e. Define Barkhausen criterion.
 - f. Name any two audio frequency oscillators and RF oscillators.
 - g. Mention the name of components used to design (i) clipper circuit (ii) clamper circuit
 - h. Define Monostable multivibrator.
 - i. Define CMRR and Slew rate of an Op-amp.
 - j. Draw the pin diagram of 555 timer and mention each pin name.

2. Answer **Any Six** Questions 6 x 5
 - a. Explain the current flow mechanism in a p-n junction under:
 - (i) No bias
 - (ii) Forward bias
 - (iii) Reverse bias condition
 - b. Differentiate between voltage and power amplifier.
 - c. Classify FETs. Draw the symbols showing current direction and name each terminal.
 - d. (i) Draw block diagram of voltage series feedback amplifier. [2]

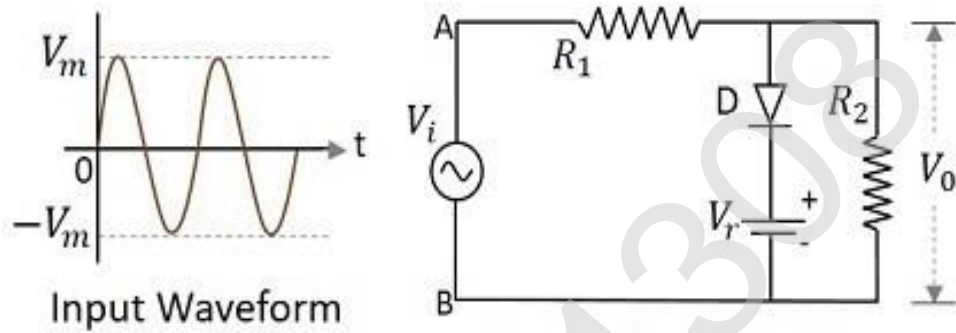(ii) Determine the voltage gain, input, and output impedance with feedback for voltage series feedback having open loop gain (A) = **100**, input resistance (R_{in}) = **10 k Ω** , output resistance (R_o) = **20 k Ω** for feedback fraction of β = **0.1**. [3]
 - e. Draw the circuit diagram of inverting and non inverting amplifier using Op-amp. Also, Compute gain of both the circuits if input resistance (R_{in}) = **1k Ω** and feedback resistance (R_f) = **10k Ω** .
 - f. Explain the working of a voltage to current convertor using Op-amp.

- g A sinusoidal signal having maximum voltage $V_m = 5V$ is applied to the clipper circuit having bias voltage $V_r = 1V$ as given below. Draw the output waveform.



- 3 With neat diagram describe the working principle of RC coupled amplifier with its frequency response curve. **10**
- 4 With neat sketch, explain the working of Class – B push pull amplifier. **10**
- 5 Explain the working of wine-bridge oscillator with circuit diagram. Write the expression for frequency of oscillation. **10**
- 6 Explain the operation of integrator and differentiator using OP-AMP with neat diagrams. **10**
- 7 Explain the operation of Astable multi-vibrator using IC-555 with a neat circuit diagram. **10**